
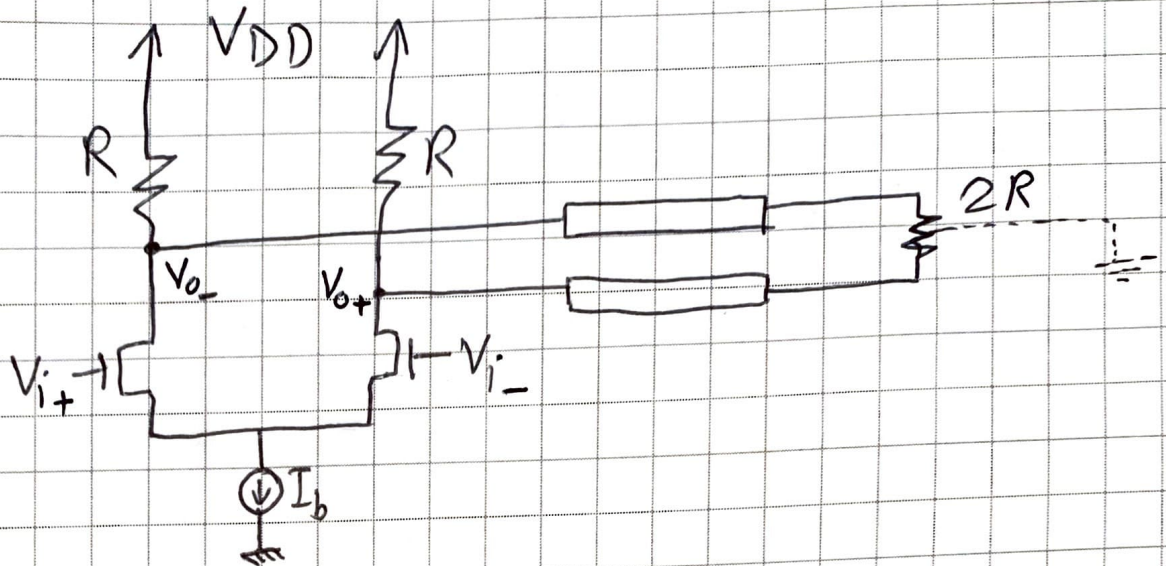


CML Tx-Driver

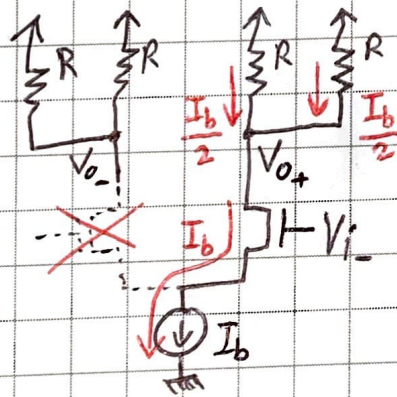

* Swing



$$V_{o-} = V_{DD}$$


$$V_{o+} = V_{DD} - I_b \left(\frac{R}{2} \right)$$

$$\therefore V_{sw, pk} = V_{o+} - V_{o-}$$

$$= \pm I_b \left(\frac{R}{2} \right)$$

$$\therefore V_{sw, pk2pk} = I_b R$$

Another way of viewing this:

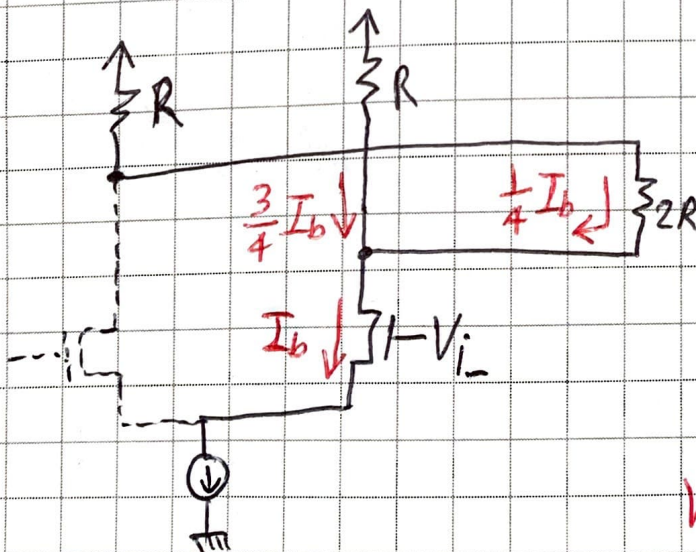


$$V_{sw, pk} = \pm \frac{1}{4} I_b \cdot 2R$$

$$\therefore V_{sw, pk2pk} = I_b R$$

V_{sw} depends on I_b
pk2pk

* Replica (for swing control)

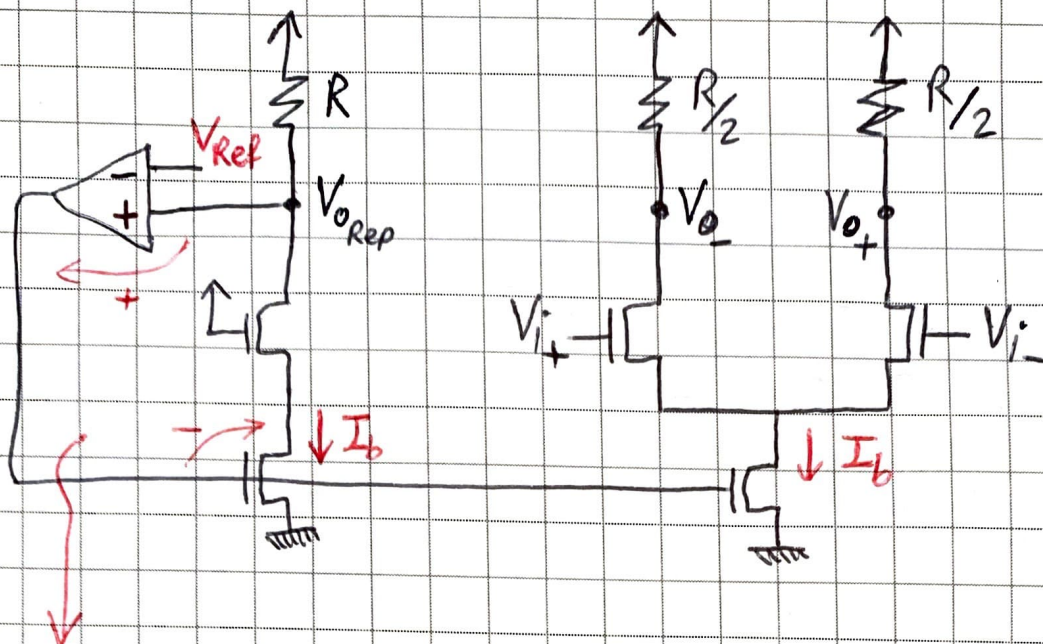

-ve feedback loop
adjusts I_b value
to keep the relationship:

$$V_{sw\text{ pk2pk}} = V_{DD} - V_{Ref}$$

$$V_{oRep} = V_{Ref} = V_{DD} - I_b R$$

$$V_{o+} = V_{DD} - \frac{1}{2} I_b R$$

$$V_{o-} = V_{DD}$$

$$V_{sw\text{ pk2pk}} = V_{DD} - V_{Ref} = I_b R$$

$V_{sw\text{ pk2pk}}$ depends on V_{Ref}