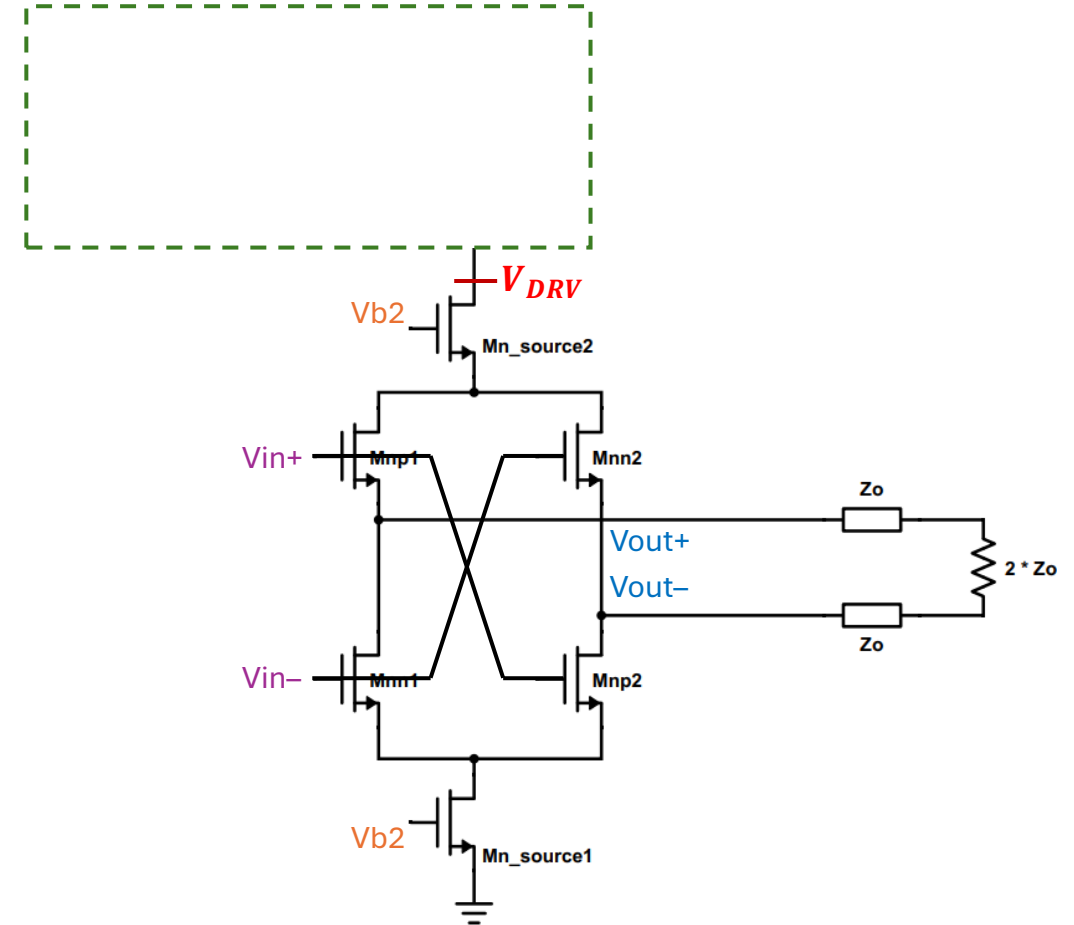


# Tx Driver – VM

Notes on devices' initial sizing

# Notes

- Start with DC Analysis.
- a) Set  $V_{IN+} = V_{dd}$  &  $V_{IN-} = \text{GND}$ .
  - b) Replace the Regulator with a DC voltage source =  $V_{DRV}$




For  $V_{Swing(pk2pk)} = 500 \text{ mV}$ :

$$V_{REF} = V_{DRV} = 500 \text{ mV}$$
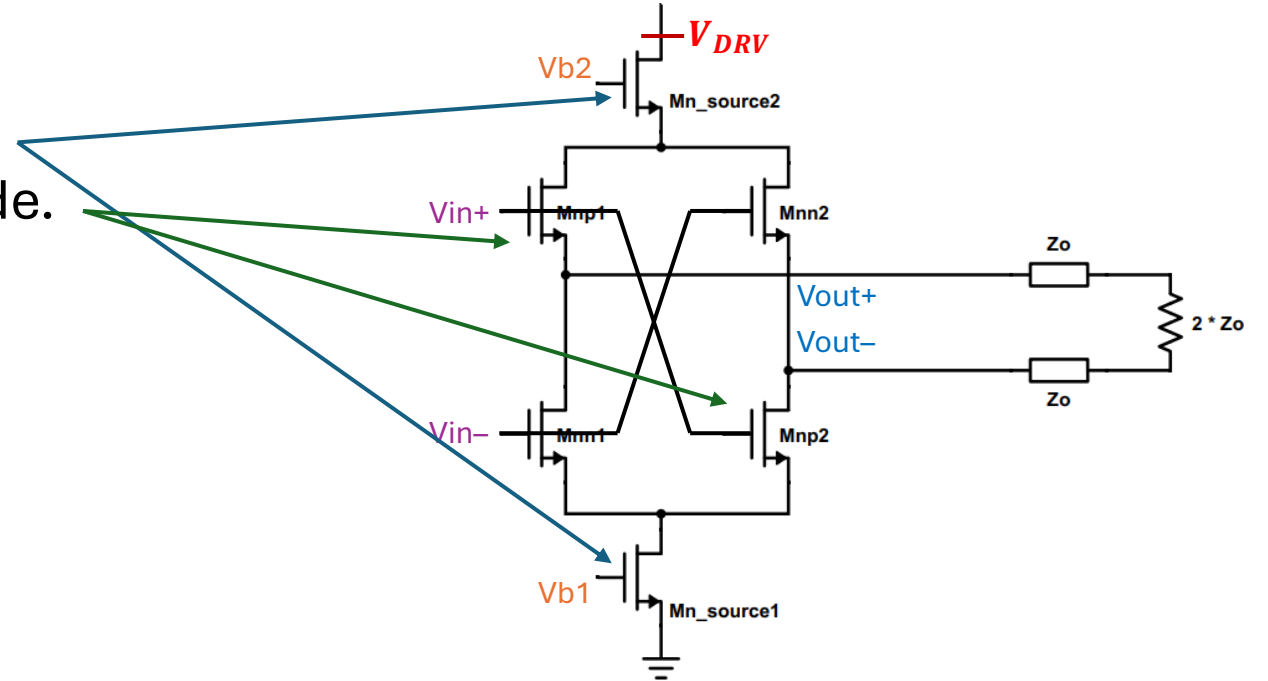
# Notes

- Start with DC Analysis.
- Source devices should be in SAT.
  - Switch (input) devices are in Triode.




# Notes

## ➤ Start with DC Analysis.

### ❖ Upper devices:

- Start with Some initial sizes for the 2 devices.
- Connect  $R = 3 \cdot Z_o = 150 \text{ Ohm}$  to  $V_{out+}$  (Connected to GND).
- Find  $V_{b2}$  that will make  $V_{out+} = \frac{3}{4} * V_{DRV}$ .

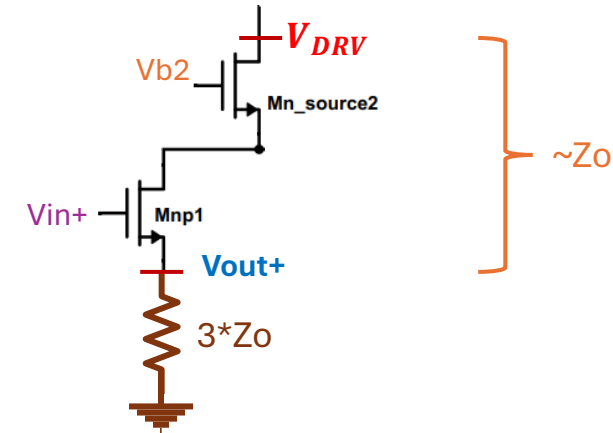


Mnp1 :	$L = L_{MIN}$	, m=100x
Mn_source2 :	$L = L_{MIN}$	, m=200x

# Notes

## ➤ Start with DC Analysis.
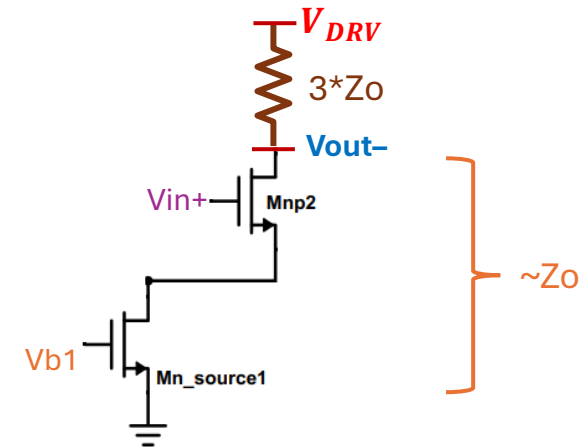
### ❖ Lower devices:

- Start with Some initial sizes for the 2 devices.
- Connect  $R = 3 \cdot Z_o = 150 \text{ Ohm}$  to  $V_{out-}$  (Connected to  $V_{DRV}$ ).
- Find  $V_{b1}$  that will make  $V_{out-} = \frac{1}{4} \cdot V_{DRV}$ .



$M_{np1}$ :	$L = L_{MIN}$	, $m=100x$
$M_{n\_source2}$ :	$L = L_{MIN}$	, $m=200x$